

Electronic Devices

Final Term Lecture - 06

Reference book:

Electronic Devices and Circuit Theory (Chapter-7)

Robert L. Boylestad and L. Nashelsky , (11th Edition)



Faculty of Engineering

American International University-Bangladesh

OBJECTIVES

- Be able to perform a dc analysis of JFET, MOSFET, and MESFET networks.
- Become proficient in the use of load-line analysis to examine FET networks.
- Develop confidence in the dc analysis of networks with both FETs and BJTs.
- Understand how to use the Universal JFET Bias Curve to analyze the various FET configurations.



GENERAL RELATIONSHIPS

- For all FETs: $I_G \approx 0A$ $I_D = I_S$
- For JFETs and Depletion-Type MOSFETs: $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$
- For Enhancement-Type MOSFETs: $I_D = k(V_{GS} - V_T)^2$
- BJT: **Linear Relationship** between I_B and I_C
- FET: **Non-linear Relationship** between V_{GS} and I_D .



COMMON FET BIASING CIRCUITS

- JFET
 - Fixed – Bias
 - Self-Bias
 - Voltage-Divider Bias
- Depletion-Type MOSFET
 - Self-Bias
 - Voltage-Divider Bias
- Enhancement-Type MOSFET
 - Feedback Configuration
 - Voltage-Divider Bias



FIXED-BIAS JFET

- The simplest biasing arrangements:

$$I_G \approx 0A \quad I_D = I_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

- For the DC analysis,
 - Capacitors are open circuits

$$I_G \cong 0A \quad V_{RG} = I_G R_G = (0A) R_G = 0V$$

- The **zero-volt drop across R_G** permits **replacing R_G by a short-circuit.**

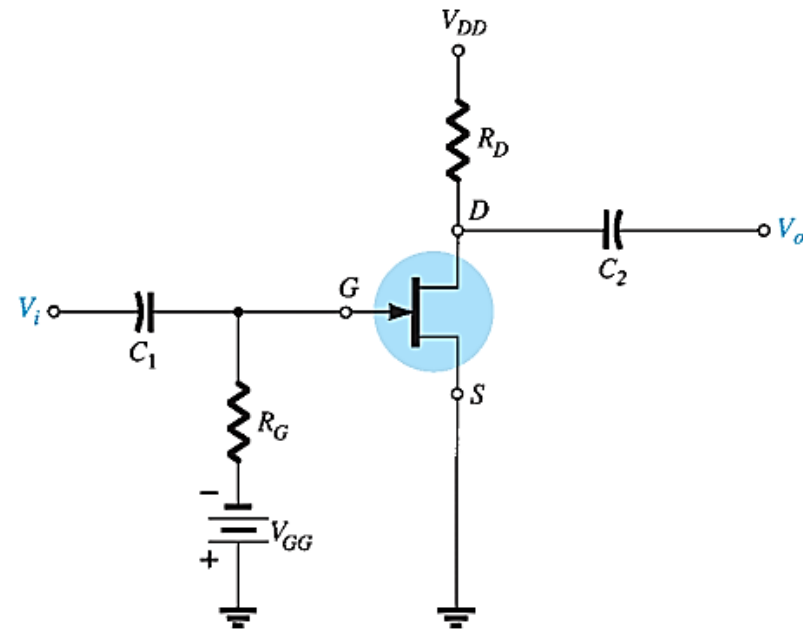


FIG. 7.1

Fixed-bias configuration.

FIXED-BIAS JFET

- Can be solved using either **Mathematical Approach** or **Graphical Approach**:

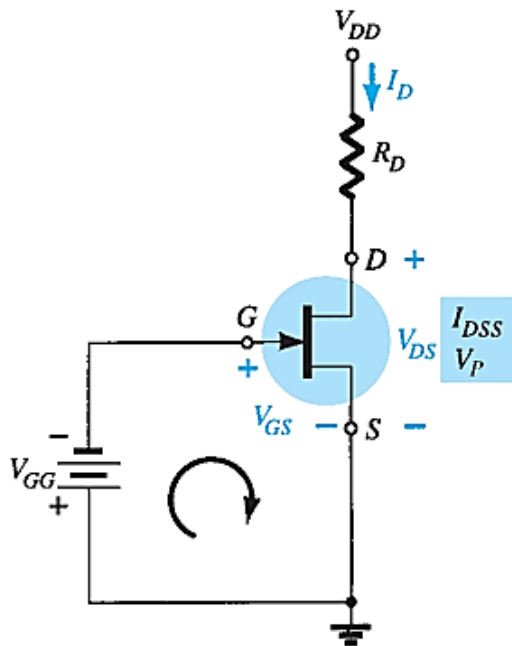


FIG. 7.2

Network for dc analysis.

Mathematical Approach

$$V_{GS} = -V_{GG}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0$$

$$V_D = V_{DS}$$

$$V_G = V_{GS}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Graphical Approach

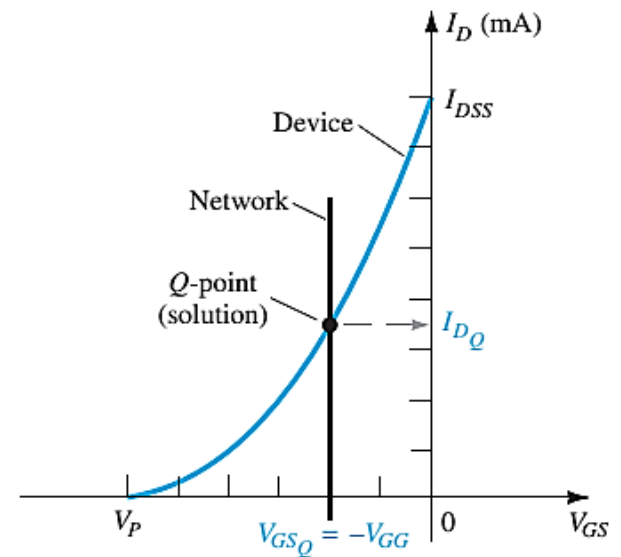


FIG. 7.4

Finding the solution for the fixed-bias configuration.

FIXED-BIAS JFET EXAMPLE

- Determine V_{GSQ} , I_{DQ} , V_{DS} , V_D , V_G , V_S .

Mathematical Approach

- $V_{GSQ} = -V_{GG} = -2 \text{ V}$
- $$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 - \frac{-2 \text{ V}}{-8 \text{ V}} \right)^2$$
$$= 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625)$$
$$= 5.625 \text{ mA}$$
- $$V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega)$$
$$= 16 \text{ V} - 11.25 \text{ V} = 4.75 \text{ V}$$
- $V_D = V_{DS} = 4.75 \text{ V}$
- $V_G = V_{GS} = -2 \text{ V}$
- $V_S = 0 \text{ V}$

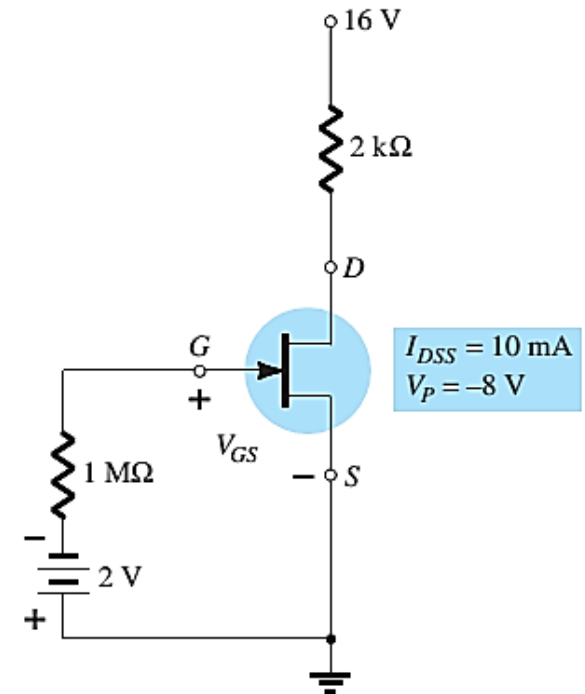


FIG. 7.6
Example 7.1.

FIXED-BIAS JFET EXAMPLE

Graphical Approach

$$V_{GS_Q} = -V_{GG} = -2 \text{ V}$$

$$I_{D_Q} = 5.6 \text{ mA}$$



$$V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega) \\ = 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$$

$$V_D = V_{DS} = 4.8 \text{ V}$$

$$V_G = V_{GS} = -2 \text{ V}$$

$$V_S = 0 \text{ V}$$

V_{GS}	I_D
0	I_{DSS}
$0.3V_P$	$I_{DSS}/2$
$0.5V_P$	$I_{DSS}/4$
V_P	0mA

 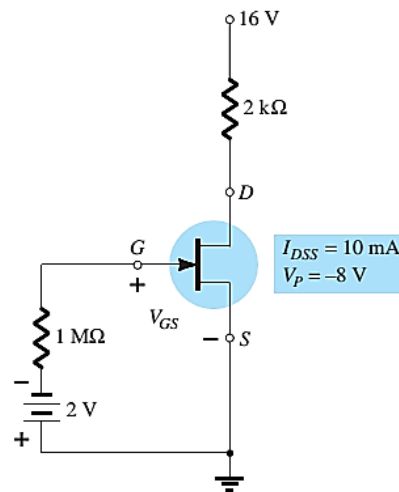

JFET: SELF-BIAS CONFIGURATION

- The self-bias configuration *eliminates the need for two dc supplies.*

$$I_G \approx 0A$$

$$I_D = I_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

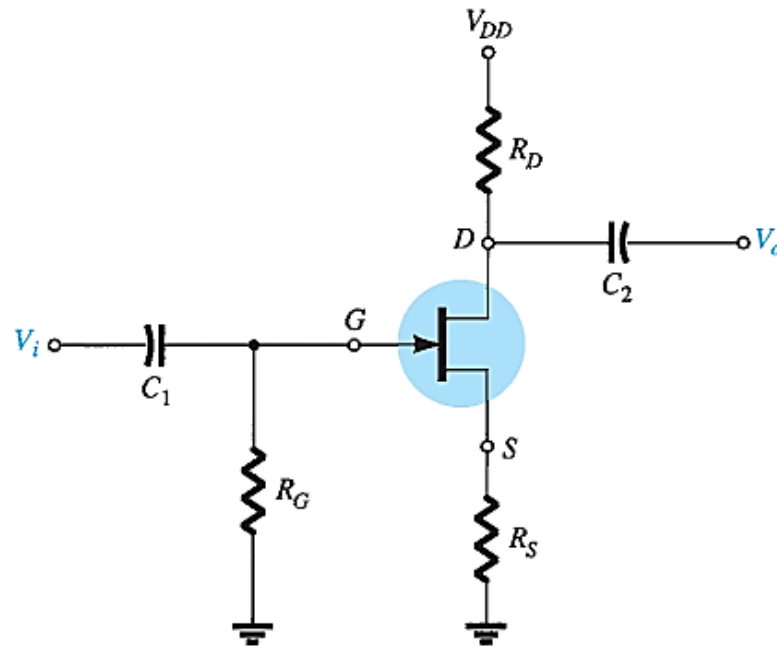


FIG. 7.8

JFET self-bias configuration.

 


FIG. 7.9

DC analysis of the self-bias configuration.

SELF-BIAS CONFIGURATION

- Can be solved using either **Mathematical Approach** or **Graphical Approach**:

Mathematical Approach

$$V_{GS} = -I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$

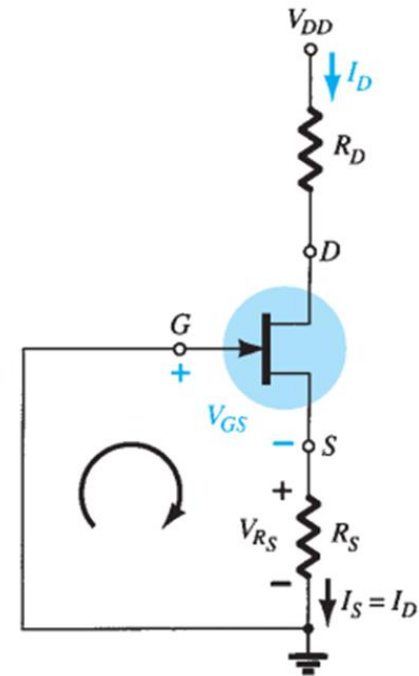


FIG. 7.9

DC analysis of the self-bias configuration.

SELF-BIAS CONFIGURATION

Graphical Approach

- Draw the device transfer characteristic using **shorthand method**.
- Draw the network load line

- Use $V_{GS} = -I_D R_S$ to draw straight line.
- First point, $I_D = 0, V_{GS} = 0$
- Second point, any point from $I_D = 0$ to $I_D = I_{DSS}$. Choose

$$I_D = \frac{I_{DSS}}{2} \text{ then}$$

$$V_{GS} = -\frac{I_{DSS} R_S}{2}$$

- The Q-point obtained at the intersection of the straight line plot and the device characteristic curve.
- The quiescent value for I_D and V_{GS} can then be determined and used to find the other quantities of interest.



SELF-BIAS CONFIGURATION

Graphical Approach

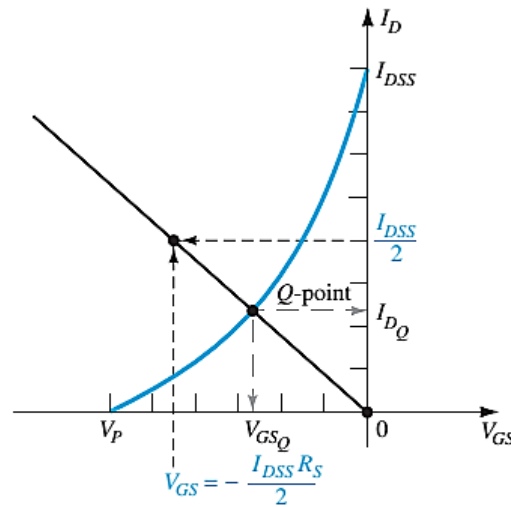


FIG. 7.11

Sketching the self-bias line.

SELF-BIAS EXAMPLE

Determine V_{GSQ} , I_{DQ} , V_{DS} , V_S , V_G and V_D .

Mathematical Approach

$$V_{GS} = -I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$

$$V_{GS} = -I_D R_S$$

$$V_{GS} = -2.6 \text{ mA} \times 1 \text{ k} \\ = -2.6 \text{ V}$$

 


FIG. 7.12
Example 7.2.

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$

$$\Rightarrow I_D = 8 \text{ m} \left(1 + \frac{I_D \cdot 1 \text{ k}}{-6} \right)^2$$

$$\Rightarrow I_D = 8 \text{ m} \left(1 - \frac{I_D \times 10^3}{6} \right)^2$$

$$\Rightarrow I_D = 8 \text{ m} \left(\frac{6 - I_D \times 10^3}{6} \right)^2$$

$$\Rightarrow I_D = \frac{2}{9} \text{ m} (6 - I_D \times 10^3)^2$$

$$\Rightarrow \frac{9}{2 \text{ m}} I_D = (6 - I_D \times 10^3)^2$$

$$\Rightarrow 4.5 \times 10^3 I_D = 36 - 2 \times I_D \times 10^3 \times 6 + I_D^2 \times 10^6$$

$$\Rightarrow I_D^2 \times 10^6 - 16.5 \times 10^3 I_D + 36 = 0$$

$$\Rightarrow I_D = \frac{-16.5 \times 10^3 \pm \sqrt{(16.5 \times 10^3)^2 - 4 \times 10^6 \times 36}}{2 \times 10^6}$$

$$\Rightarrow I_D = 2.59 \text{ mA} \text{ or } 13.95 \text{ mA}$$

Since, $I_{DSS} = 8 \text{ mA}$, so, $I_D = 13.95 \text{ mA}$ is not acceptable.
 $\therefore I_D = 2.6 \text{ mA}$

End of Lecture-6

