

AMERICAN INTERNATIONAL UNIVERSITY-BANGLADESH (AIUB) FACULTY OF SCIENCE & TECHNOLOGY ELECTRONIC DEVICES LAB

Spring 2022-2023

Section:U

LAB REPORT OEL:

Performance analysis of a common source (CS) E-MOSFET amplifier circuit by varying the loads and justification of the analysis with respect to simulated and experimental data (followed by the given constraints).

Supervised By

DR. MOHAMMAD ALIF ARMAN

GROUP NO: 02

Name	ID
1.FARJANA YESMIN OPI	22-47018-1
2.RUBAET RAZ RISHAD	22-46377-1
3. MD. ASIKUR RAHMAN TAJ	22-46284-1
5. MD RIFAT ALI	22-46131-1
4.SUMAIYA SHARMEEM SHAILY	22-46501-1

Date of Submission: 14th MAY, 2023

Title:

Performance analysis of a common source (CS) E-MOSFET amplifier circuit by varying the loads and justification of the analysis with respect to simulated and experimental data (followed by the given constraints).

Objective:

Design a common source E-MOSFET amplifier circuit and analyze the gain with varying the loads. Finally, a complete analysis will be expected with respect to experimental and simulated data.

Literature review:

MOSFET devices belong to the group of Insulated Gate Field Effect Transistor (IGFETs). MOSETs like all other IGFETs has three terminals, which are called Gate (G), Source (S), and Drain (D). In PMOS, the body terminal is held at the most positive voltage in the circuit and in NMOS, it is held at the most negative voltage in the circuit.

There are four types of MOSFETs: enhancement n-type MOSFET, enhancement p-type MOSFET, depletion n-type MOSFET, and depletion p-type MOSFET. If the channel between the drain and the source is an induced channel, the transistor is called enhancement transistor. Throughout the handout, we will concentrate on analyzing the enhancement type MOSFET. If we put the drain and source on ground potential and apply a positive voltage to the gate, the free holes (positive charges) are repelled from the region of the substrate under the gate (channel region) due to the positive voltage applied to the gate. The holes are pushed away downwards into the substrate leaving behind a depletion region. At the same time, the positive gate voltage attracts electrons into the channel region. When the concentration of electrons near the surface of the substrate under the gate is higher than the concentration of holes, an n region is created, connecting the source and the drain regions. In the case of an enhancement type NMOS transistor the threshold voltage is positive, whereas an enhancement type PMOS transistor has a negative threshold voltage. So, in order for the current to flow from drain to source, the condition that should be satisfied is $V_G > V_{th}$, where V_G is the gate voltage and V_{th} is the minimum voltage required to form a

channel between drain and source so that carriers can ow through the channel. By changing the applied gate voltage, we can modulate the conductance of the channel.

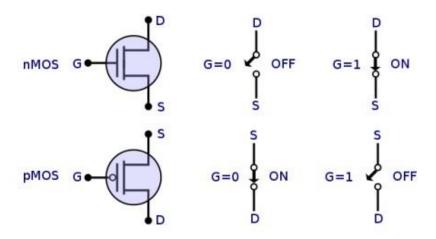


Figure: Symbols for enhancement NMOS and PMOS transistors

Apparatus:

Apparatus	Quantity
MOSFET	1
Trainer board	1
Resistors	8
Oscilloscope	1
Multimeter	1
Signal Generator	1
Capacitors	1
DC Power Supply	1

Experimental data table:

Table 1

V _{DD}	$\mathbf{V}_{\mathbf{D}}$	V _{DD} -V _D	$I_D = (V_{DD} - V_D) / R_D$	Vds
10 V	95.7 mV	9.91 V	6.67 mA	9.98 V

Table 2

Load resistor	Input voltage	Output voltage	Gain
1k	400 mV	3.9 mV	00.00975
4.7k	420 mV	10.1 mV	0.024
10k	420 mV	9.4 mV	0.022
100k	420 mV	13.1 mV	0.031


Simulated data table:


Table 3


V _{DD}	V_{D}	V _{DD} -V _D	$I_D = (V_{DD} - V_D) / R_D$	Vds
10V	7.966 V	2.004	5.311 mA	10 V

Table 4


Load resistor	Input voltage	Output voltage	Gain
1k	16.6V	9.91mV	0.597
4.7k	16.7V	43.7mV	2.62
10k	16.03V	95.2mV	5.94
100k	16.2V	258.9mV	15.98

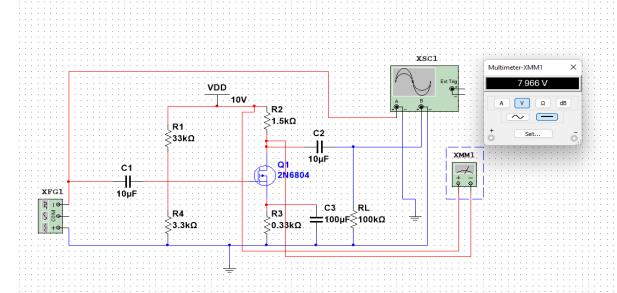

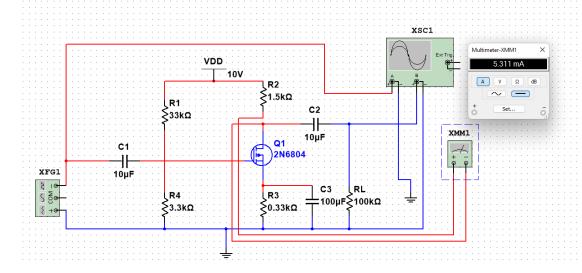


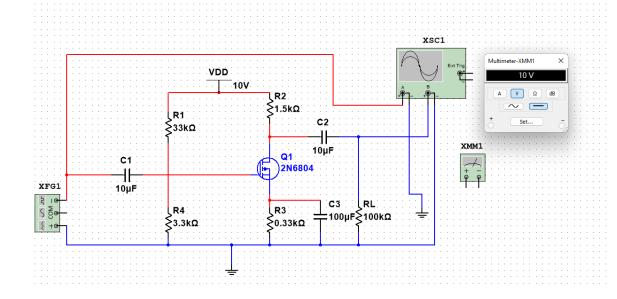


For load resistance 1 kilo ohm:

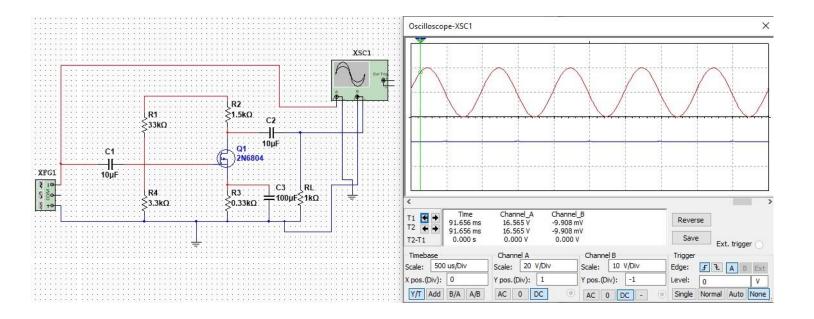


For load resistance 4.7 kilo ohm:

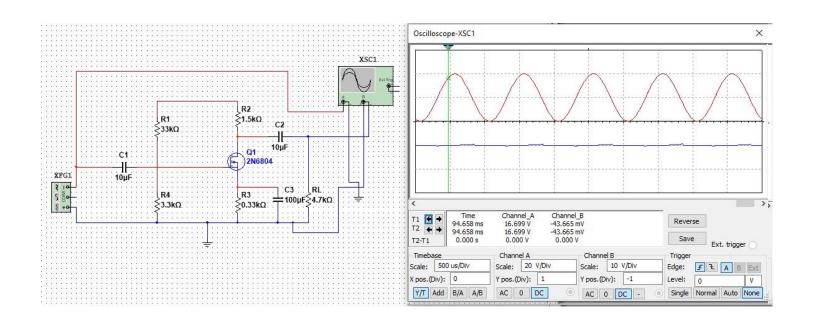


For load resistance 10 kilo ohm:

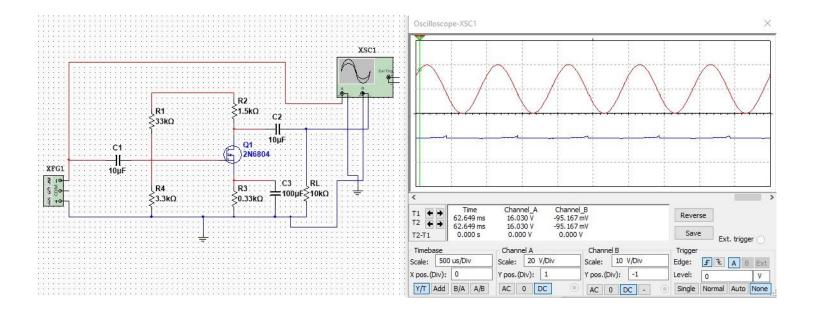


For load resistance 100 kilo ohm:

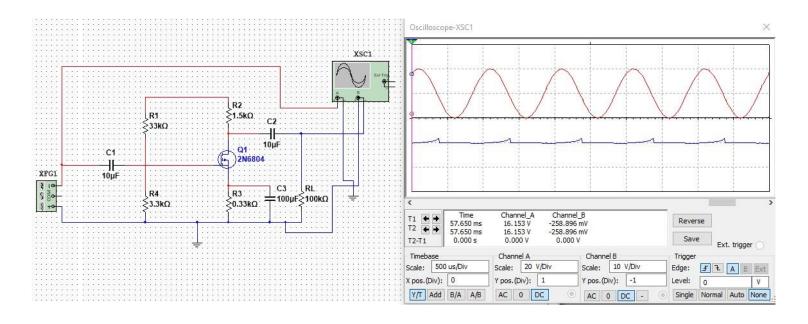

Practical images:

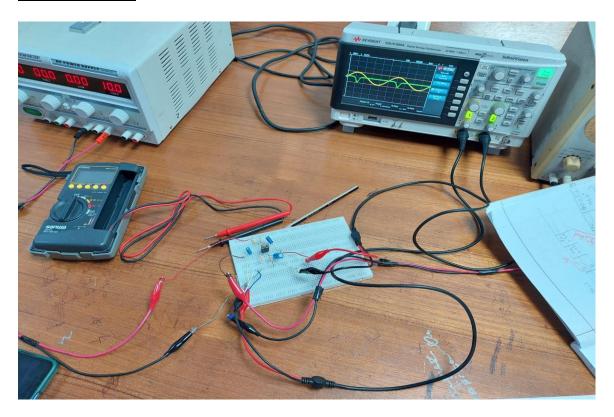

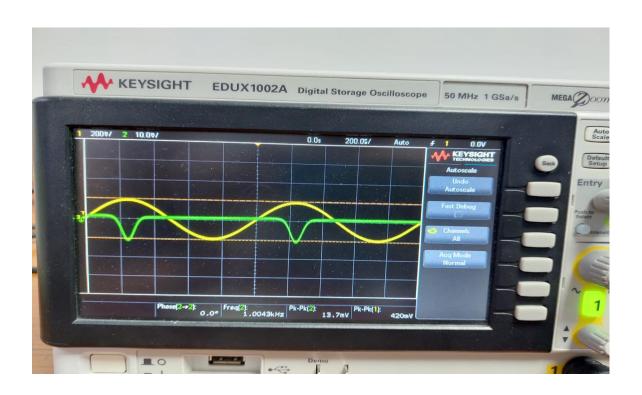

Discussion:

In this experiment the concept of E-MOSFET common source small signal amplifier was illustrated and the characteristics and applications were discussed. After that the circuit was implemented on the trainer board to determine the voltage gain, input and output voltages by using DC and AC analysis and to investigate the input and output waveforms of CS amplifier circuit. While AC analysis we faced some difficulties in calibrating the oscilloscope but with the help of our lab assistant instructor the issue was fixed. Both of the table was filled up carefully. Then with the help of NI Multisim software the implemented circuit was simulated and compared with themeasured value. Some differences were noticed but they are negligible. These negligible errorsmight be occurred due to unstable power sources used in the lab or fluctuation of Oscilloscope. Since there is no big difference between measured value and simulated value, it can be said that the main objectives for this experiment is accomplished.

References:

- [1] Electronics Tutorials, "MOSFET Amplifier Circuit using an Enhancement MOSFET", https://www.electronics-tutorials.ws/amplifier/mosfet-amplifier.html
- [2] Libretexts, "MOSFET Common Source A mplifiers",

https://eng.libretexts.org/Bookshelves/Electrical_Engineering/Electronics/Book% 3A_Semiconductor_Devices_-

<u>Theory and Application (Fiore)/13%3A MOSFET Small Signal Amplifiers/13.2</u> %3A_M OSFET_Common_Source_Amplifiers

- [3] American International University Bangladesh AIUB Electronic Device Lab Manual.
- [4] Electronics Tutorials: <u>Amplifier Distortion in Transistor</u> <u>Amplifiers (electronics-tutorials.ws)</u>